

Solution Set 3


Exercises 12.16, 12.17, 12.18, 12.19, 12.20, 12.21, 12.22, 12.23, 12.24

12.16
 $B9_{16}$
 $= 10111001$


CL	Q ₇	Q ₆	Q ₅	Q ₄	Q ₃	Q ₂	Q ₁	Q ₀	D
0	0	0	0	0	0	0	0	0	1
1	1	0	0	0	0	0	0	0	0
2	0	1	0	0	0	0	0	0	0
3	0	0	1	0	0	0	0	0	0
4	1	0	0	1	0	0	0	0	0
5	1	1	0	0	1	0	0	0	0
6	1	1	1	0	0	1	0	0	0
7	0	1	1	1	0	0	1	0	0
8	1	0	1	1	1	0	0	1	0

12.17 LET $Q_1 Q_2 Q_3 Q_4$ BE THE OUTPUT STATE OF THE SHIFT REGISTER.

(a) $F_{16} = 1001$

 


(b) $A_{16} = 1010$

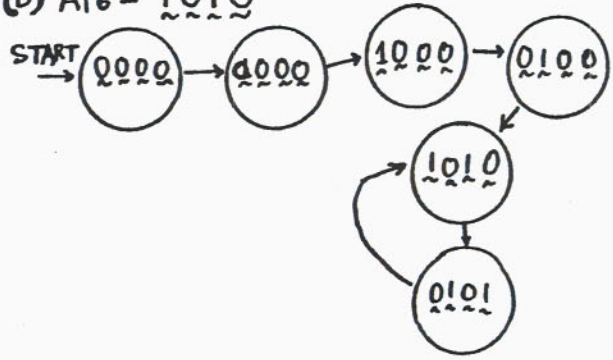

(ONLY TWO STATES ARE REPEATED, SINCE 1010 HAS THE REPEATED PATTERN 10)


c) $F_{16} = 1111$

 


12.18. a)

N	I_N	Q_{1N}	Q_{2N}	Q_{3N}	Q_{4N}
0	0	1	0	0	0
1	0	0	1	0	0
2	0	0	0	1	0
3	1	0	0	0	1
4	0	1	0	0	0

(repeats)

 


12.19

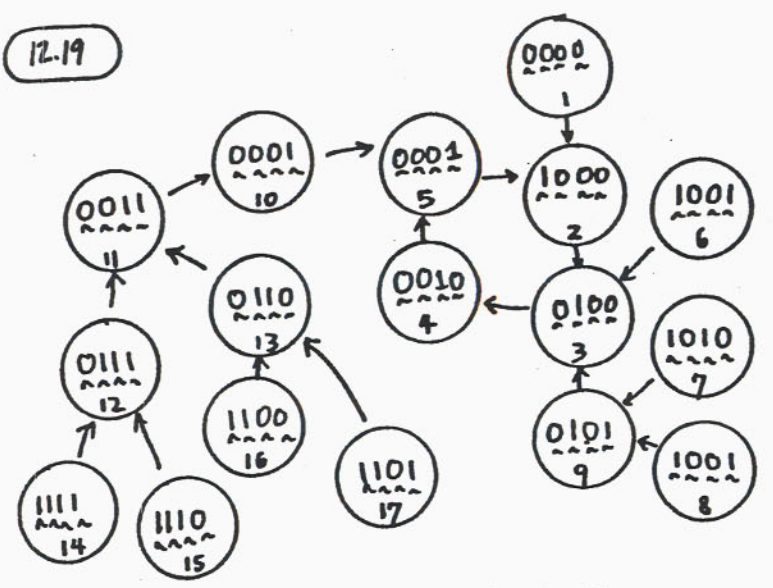

THE LIMIT CYCLE IS 2-3-4-5.

 
12.20 (a) Add a decoder to the outputs;
 FOR INSTANCE




GIVES AN
 OUTPUT OF 1
 EACH TIME THE
 COUNTER RETURNS
 TO STATE 5.

ALTERNATIVELY, ONE COULD SIMPLY USE \underline{I}
 AS THE OUTPUT, SINCE I GOES TO ONE
 EVERY TIME THE SYSTEM PASSES THROUGH
 STATE 5.

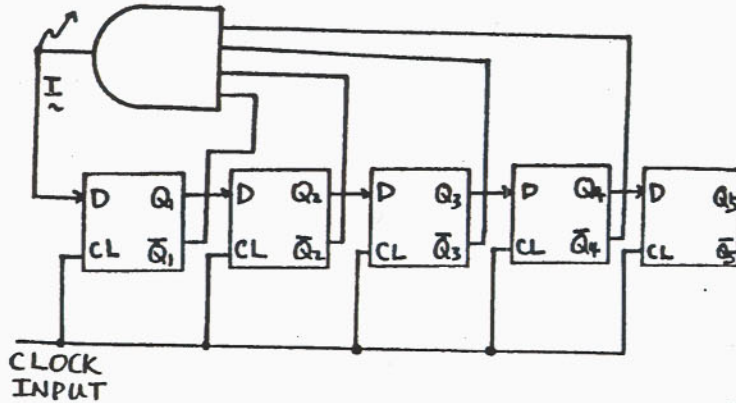(b) NOW A 4-INPUT AND GATE SHOULD
 BE USED INSTEAD. TAKE \underline{I} AS THE OUTPUT.




12.21 THE LOGIC CIRCUIT IS AS FOLLOWS:

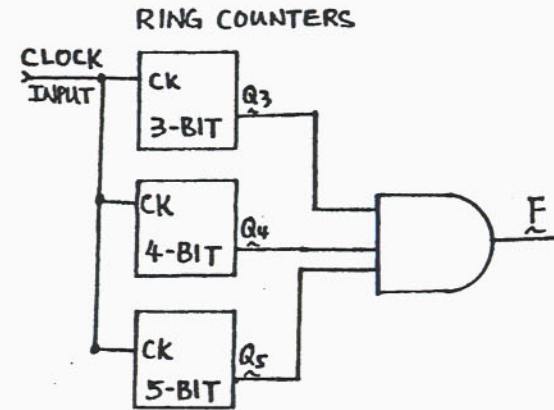


THE THREE RING COUNTERS GIVE AN OUTPUT OF $\underline{1}$ AT INTERVALS OF 3, 4 AND 5 CLOCK PULSES
 RESPECTIVELY. SO \underline{F} WOULD BE $\underline{1}$ AT AN
 INTERVAL OF $3 \times 4 \times 5 = 60$ CLOCK PULSES.
 ALSO THE NUMBER OF FLIP-FLOPS USED = 12

12.22

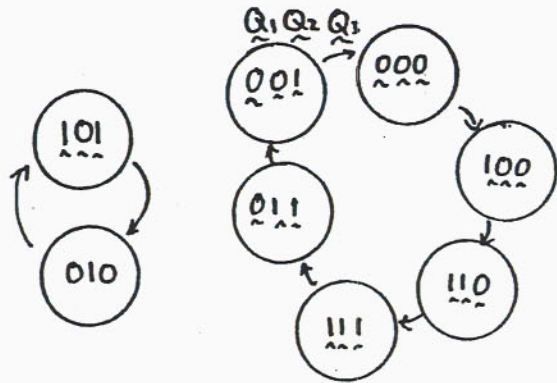


THEREFORE FROM THE STATE DIAGRAM, THERE ARE TWO LIMIT CYCLES. SINCE THERE ARE 6 STATES IN THE LARGER LIMIT CYCLE, AFTER 6 CLOCK PULSES, THE SYSTEM ALWAYS RETURNS TO ITS ORIGINAL STATE. SO IF WE USE AN AND GATE WITH Q_1, Q_2, Q_3 AS INPUTS, ITS OUTPUT WOULD GIVE A $\frac{1}{6}$ EVERY 6 CLOCK PULSES. THUS WE HAVE A DIVIDE-BY-SIX COUNTER.


12.23

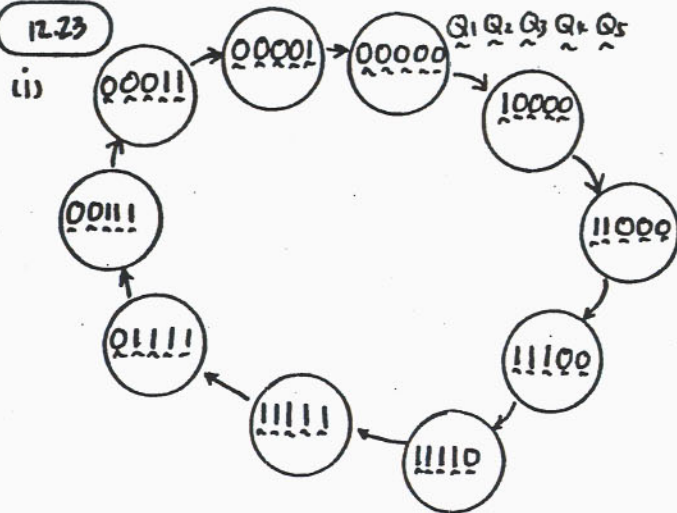


(ii)

 


(iii)

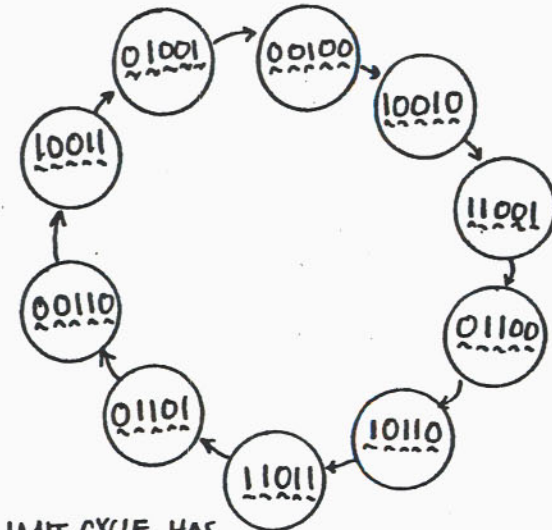


THIS LIMIT CYCLE HAS ONLY 2 STATES:

 

 
12.24 (a) $\underline{A} = 1$; $\underline{D}_1 = \overline{Q}_2$; $\underline{D}_2 = Q_1$



 
(b) $\underline{A} = 0$; $\underline{D}_1 = Q_2$; $\underline{D}_2 = \overline{Q}_1$



(c) (i) $\underline{A} = 0$

 

(ii) $\underline{A} = 1$

 

(d) THE OUTPUTS Q_1 AND Q_2 ARE TWO SQUARE WAVES. WHEN $A=0$, Q_2 LEADS Q_1 IN PHASE BY 90° . WHEN $A=1$, Q_2 LAGS Q_1 BY 90° . (THE CIRCUIT IS USED TO DRIVE A STEPPING MOTOR - SEE FIG. 17.32. CHANGING A FROM 1 TO 0 REVERSES THE MOTOR. ■