

Solution Set 6

Exercises 4.3, 4.4, 4.8, 4.9, 4.12, 4.14, 4.16, 4.19, 4.32, 4.33, 4.36, 4.39, 9.3, 9.7, 9.27, 9.30

4.3 FROM THE LEFT SIDE OF THE CIRCUIT

$$i_1 = \frac{10}{R_1} = \frac{10}{10k} = 1mA$$

FROM THE RIGHT SIDE OF THE CIRCUIT


$$i_2 = \beta i_1 = 100 (1mA) = \underline{100mA}$$

4.4 OBVIOUSLY, FROM THE RESULT OF


LAST PROBLEM, $i_2 = 1A$

$$\therefore V = i_2 R_2 = 1000 (1) V = \underline{1000V}$$

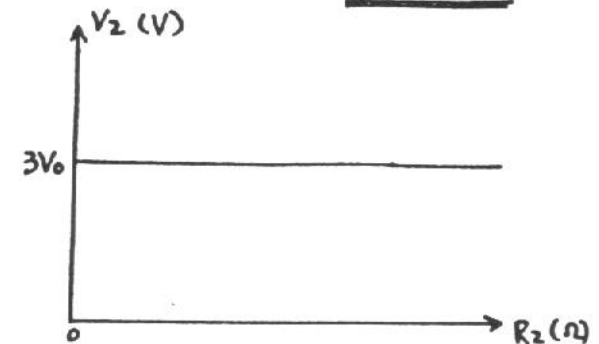4.8 (a) $V_2 = \mu V_1 = \mu V_0 = \underline{3V_0 \text{ VOLTS}}$




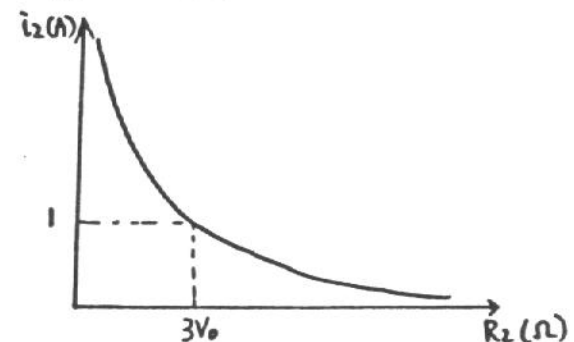(b) $i_2 = \frac{\mu V_1}{R_2} = \frac{3V_0}{R_2} A$



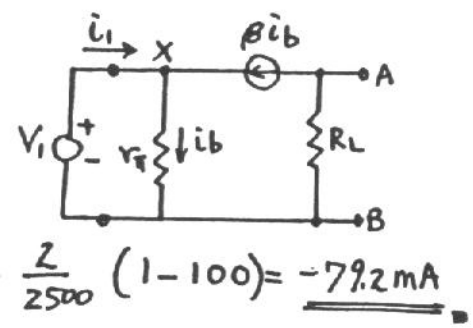
4.9

KCL AT X
 $i_1 = i_b - \beta i_b$
 $= i_b(1 - \beta)$
 $= \frac{V_L}{r_\pi}(1 - \beta) = \frac{2}{2500}(1 - 100) = -79.2 \text{ mA}$



4.12 (i) FOR V_{oc}


$V_{oc} = r_m \bar{i}_1$
 KCL AT NODE X

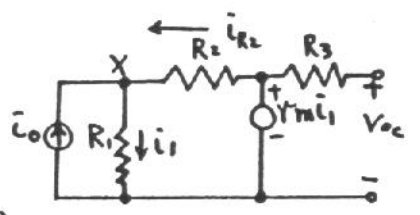

$\bar{i}_o - \bar{i}_1 R_1 + \bar{i}_2 R_2 = 0$
 $\Rightarrow \bar{i}_o - \bar{i}_1 R_1 + \frac{r_m \bar{i}_1 - \bar{i}_1 R_1}{R_2} = 0$
 $\Rightarrow \bar{i}_1 = \frac{\bar{i}_o R_2}{R_1 + R_2 - r_m}$
 $\Rightarrow V_{oc} = \frac{\bar{i}_o r_m R_2}{R_1 + R_2 - r_m}$

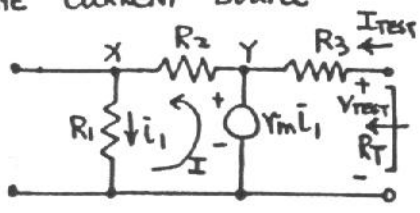(ii) FOR R_T , ZERO THE CURRENT SOURCE (INDEPENDENT).

KVL AROUND LOOP I
 $r_m \bar{i}_1 = (R_1 + R_2) \bar{i}_1$
 IF $r_m \neq R_1 + R_2$
 IS ASSUMED, \bar{i}_1 MUST BE ZERO.



THEREFORE Y IS EFFECTIVELY GROUNDDED.

4.14 THE COMPLETE CIRCUIT IS SHOWN BELOW.


KVL FOR THE RIGHT SECTION:

$-\bar{i}_L(R_L + R_p) - \mu V_{gc} = 0$
 $\Rightarrow \bar{i}_L = \frac{-\mu V_{gc}}{R_L + R_p}$

$V_{gc} = V_s$

$\Rightarrow \bar{i}_L = -\frac{\mu V_s}{R_L + R_p}$

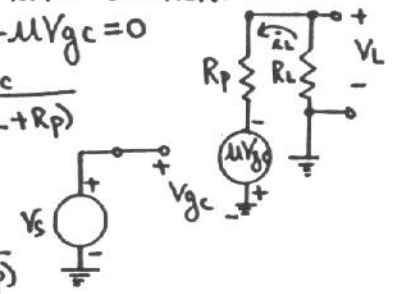$\Rightarrow V_L = -\bar{i}_L R_L$
 $= \frac{\mu R_L V_s}{R_L + R_p}$




4.16 (a) $V_1 = Z_{11} i_1 + Z_{12} i_2$
 $V_2 = Z_{21} i_1 + Z_{22} i_2$

FOR FIG 4.9(b)

$V_1 = i_1 R_1$

$V_2 = i_2 R_0 + A i_1 R_1$

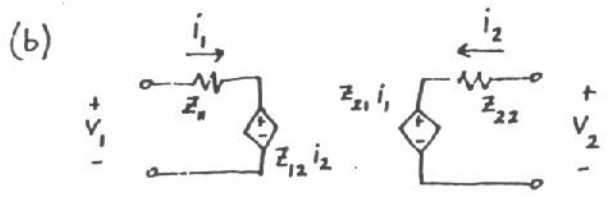THIS CAN BE PUT INTO THE DESIRED FORM IF $Z_{11} = R_1$, $Z_{12} = 0$, $Z_{21} = A R_1$, $Z_{22} = R_0$.




4.19 THIS IS GIVEN BY LAST PROBLEM

$$V_i = V_{TEST} \text{ AND } I = I_{TEST} = \frac{V_i}{R_o + (1+A)R_i}$$

$$\begin{aligned} \therefore \text{INPUT RESISTANCE } R_i' &= \frac{V_{TEST}}{I_{TEST}} = \frac{V_i}{V_i / [R_o + (1+A)R_i]} \\ &= \underline{R_o + (1+A)R_i} \end{aligned}$$

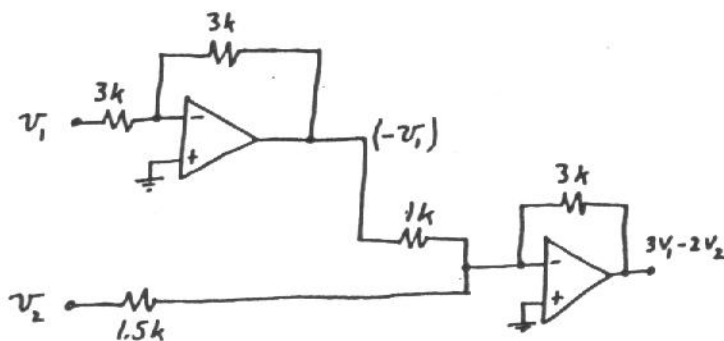4.32 USE AN INVERTING AMP FOLLOWED BY A SUMMING AMP:



4.33 WE HAVE TO PROVIDE A HIGH INPUT RESISTANCE OR VOLTAGE WILL BE LOST IN THE VOLTAGE DIVIDER COMPOSED OF R_T AND R_i' .



4.36 TO FIND V_{OUT} , THE IDEAL OP-AMP TECHNIQUE MAY BE USED.

NODE EQ. AT A (ASSUMING $v_{(-)} = v_{(+)}$ AND NO CURRENT FLOWS INTO THE (-) TERMINAL):

$$\frac{V_s}{R_1} + \frac{V_s - V_B}{R_{F1}} = 0 \Rightarrow V_B = \left[\frac{1}{R_1} + \frac{1}{R_{F1}} \right] R_{F1} V_s$$

NODE EQ. AT C (ASSUMING NO CURRENT FLOWS INTO (-) TERMINAL):


$$\frac{V_C - V_B}{R_2} + \frac{V_C - V_{OUT}}{R_{F2}} = 0$$

BY THE IDEAL OP-AMP ASSUMPTIONS, $V_C = V_{(-)} = V_{(+)} = 0$

$$\text{THUS } V_B = -\frac{R_2}{R_1} V_{OUT}$$

THEN, EQUATING THE TWO EXPRESSIONS FOR V_B AND SOLVING FOR V_{OUT} ,
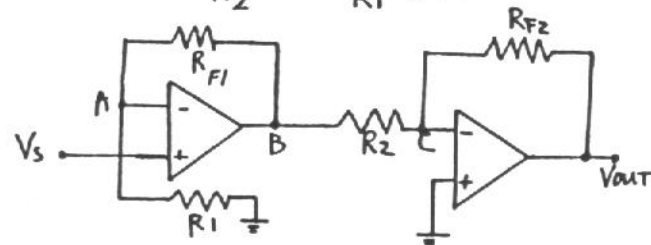
$$V_{OUT} = \frac{R_{F2}}{R_2} \left[1 + \frac{R_{F1}}{R_1} \right] V_s$$



4.39 SUMMING CURRENTS ENTERING THE (-) NODE,

$$I_0 e^{qV_{OUT}/kT} + V_{IN}/R_1 = 0$$

(WHERE WE HAVE USED THE FACT THAT $V_{(-)} = 0$, DUE TO IDEAL OP-AMP ASSUMPTIONS.)
HENCE


$$V_{OUT} = \frac{kT}{q} \ln \left(-\frac{V_{IN}}{I_0 R_1} \right)$$

THIS USEFUL CIRCUIT IS CALLED A "LOGARITHMIC AMPLIFIER."

9.3 (a) $A' = -\frac{10^5 (1000)}{(10^5 + 1)(1000) + 1000} = -0.9999800$

(b) $A' = -\frac{(1.1 \cdot 10^5)(1000)}{(1.1 \cdot 10^5 + 1)(1000) + 1000} = -0.9999818$

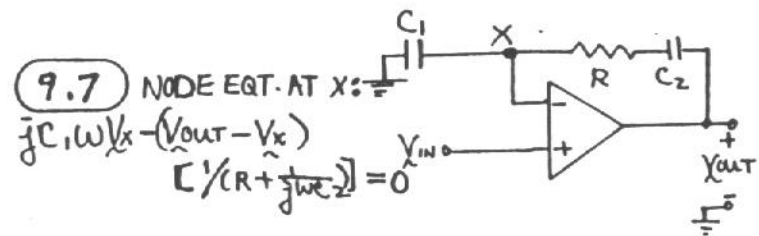(c) THE POINT IS THAT THANKS TO THE FEEDBACK, THE AMPLIFICATION OF THE CIRCUIT IS ALMOST COMPLETELY UNAFFECTED ($1.8 \times 10^{-4} \%$) BY A 10% VARIATION IN A .




SINCE $V_{(+)} = V_{(-)} = V_{IN} = V_X$,

$$V_{IN} \left[j\omega C_1 + \frac{1}{R} + \frac{1}{j\omega C_2} \right] = \frac{V_{OUT}}{R + \frac{1}{j\omega C_2}}$$

$$\Rightarrow V_{OUT} = V_{IN} \left[1 + j\omega C_1 \left(R + \frac{1}{j\omega C_2} \right) \right]$$

$$= V_0 \left[1 + j\omega C_1 \left(R + \frac{1}{j\omega C_2} \right) \right]$$


12.27

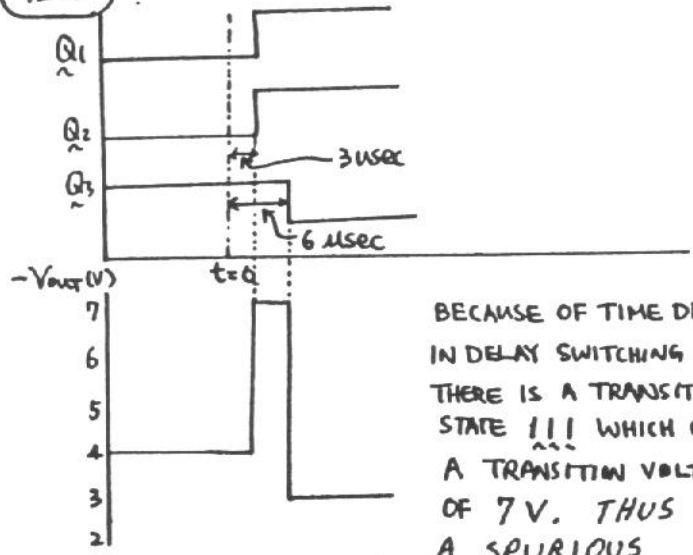

BECAUSE OF TIME DIFFERENCE IN DELAY SWITCHING TIME, THERE IS A TRANSITION STATE !!! WHICH CREATES A TRANSITION VOLTAGE OF 7V. THUS A SPURIOUS 7-V PULSE APPEARS IN THE OUTPUT.

THIS SPURIOUS OUTPUT IS KNOWN AS A "GLITCH".

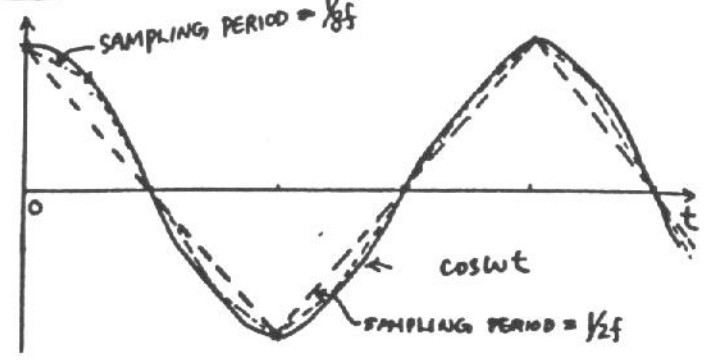12.30 a) ASSUME THE THE COSINE FUNCTION IS $\cos \omega t$



(b) THE GREATEST ERROR OCCURS AT THE PLACE THE CURVATURE (2ND DERIVATIVE) IS LARGEST. FOR THE COSINE THIS IS NEAR $\theta = 0$. LET THE SAMPLING INTERVAL BE $\frac{2\pi}{Nf}$. THE MAX ERROR IS THEN AT THE TIME $\frac{\pi}{Nf}$:

$$\text{ERROR} = \cos \frac{\pi}{N} - \left[\frac{1 + \cos \frac{2\pi}{N}}{2} \right]$$

USING $\cos \epsilon \cong 1 - \frac{1}{2} \epsilon^2$ (VALID FOR $\epsilon \ll 1$) THIS BECOMES

$$\text{ERROR} \cong \frac{\pi^2}{2N^2} = 3.9 \cdot 10^{-3}$$

FROM WHICH

$$N \cong 36$$