


Digital Basics

Analog vs digital

Analog quantities - continuous range of values all of which are equally significant. Usually associated with natural processes, e.g. pressure, temp, pH - - -


Digital quantities - discrete and quantized values used to convey information.

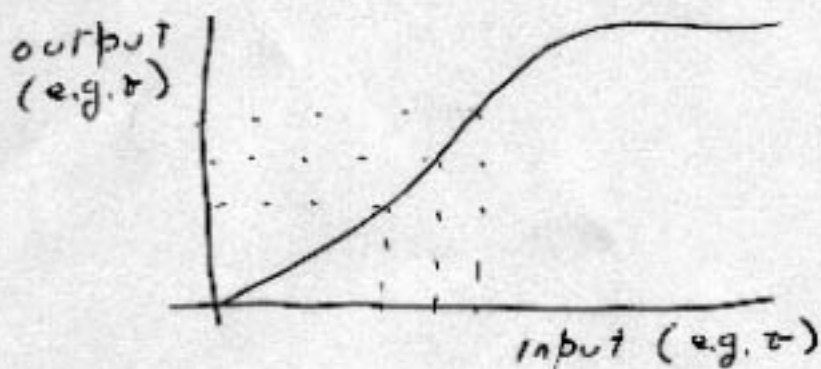Consider some device or system that has terminal characteristics as:



as an analog system each point on the characteristic has equal significance


as a digital system

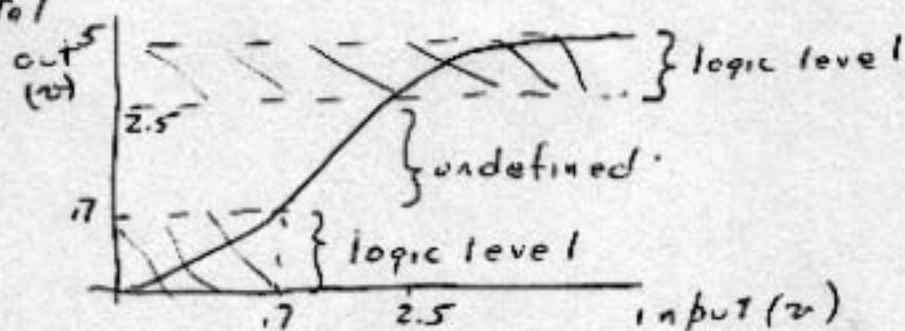

Discrete: only two values

Quantized: within the ranges shown

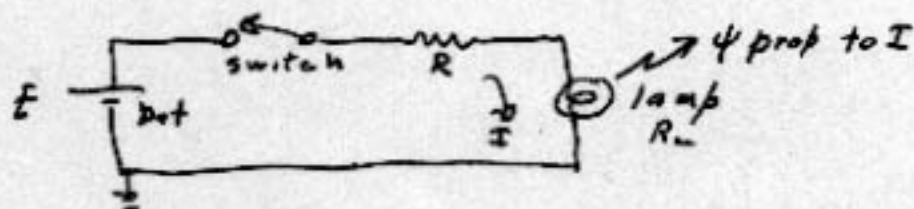Consider simple system ^{from} with two viewpoints:




as an analog system Ohms law applies when switch is ^{closed}

$$I = \frac{E}{R + R_L} \quad \text{and} \quad \psi = K \cdot I$$

depending on E, R, R_L , lamp is dim to bright

as a digital system

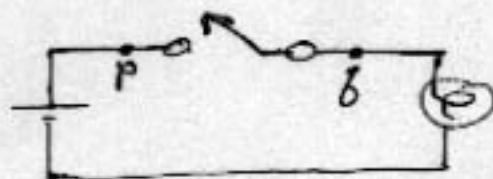Assume the battery voltage and R values are such that when switch is closed the lamp will be lit. Then only interested in whether or not the lamp is lit or alternately whether or not there is a connection between points p, q , i.e. what is the state?



Most direct way of describing the state is by means of a "word statement". There will be a connection between p, q (which implies lamp will be lit) when the switch is closed.

More compactly - define "states"

$$A \equiv \text{state of switch} = 0 \text{ if open} \\ = 1 \text{ if closed}$$


$$S \equiv \text{state of connection } p, q = 0 \text{ if no connection (lamp 0)} \\ = 1 \text{ if a connection (lamp 1)}$$

then can summarize the word statement in a little table called a "truth table"

A	S
0	0 ⇒ switch open, no connection, lamp off
1	1 ⇒ switch closed, a connection, lamp on

Things get more interesting when add more switches and/or different connections,

e.g. switches in series

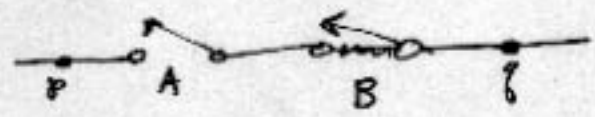


Word statement: there will be a connection between p + q (lamp will be lit) when switches A and B are both closed. (Key word is "and").

T. Table form

A	B	S
0	0	0 lamp off
0	1	0
1	0	0
1	1	1 lamp on

switches in parallel

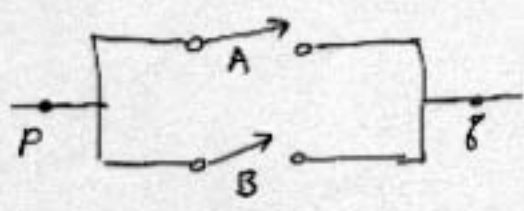

word: connection when either switch A or B is closed.

(Key word is "or")

A	B	S
0	0	0 lamp off
0	1	1 " on
1	0	1
1	1	1

Consider a "ganged" switch pair (ganged implies if one side is closed, other side is open)



could label as "B" but has special relationship to A so label as \bar{A}


word: there is always a connection

T.T.

A	\bar{A}	S
0	1	1
1	0	1


Key word is "inversion"

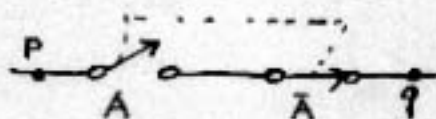what if had series ganged?
(then never a connection)



Consider combinations of above types

1)

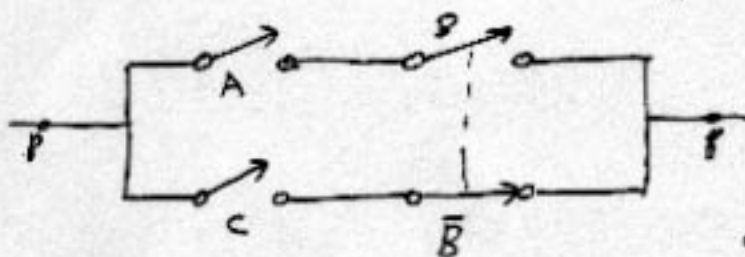

Word: Connection if

1. A closed and B closed + C doesn't matter

or 2. B open and C closed + A doesn't matter.

T.T.


A	B	C	S
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

← B open, C closed, A doesn't matter

Note: filling in T.T. forces all circuit conditions to be examined.

← A closed, B closed, C doesn't matter

2) Develop word statement and T.T. for:

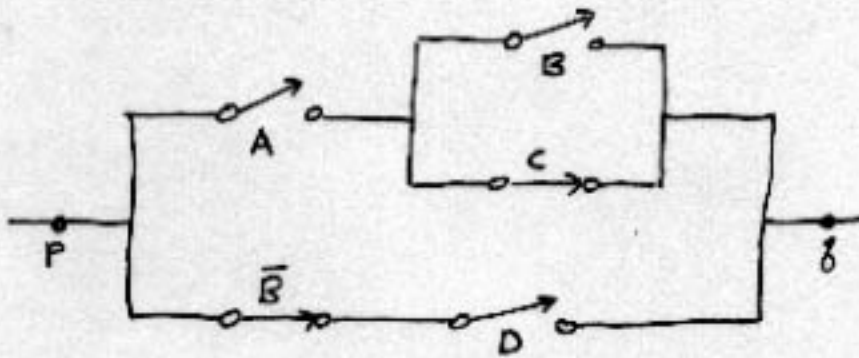

Home exercise

A	B	C	D	S
0	0	0	0	0
				etc

Functions of Binary Variables

Actual mechanical switches have been used for a long time to control various processes. Semiconductor substitutes are now used instead.

Modern development of the theory generally conceded to begin with Claude Shannon in his MIT Masters thesis "A Symbolic Analysis of Relay and Switching Circuits" (1938) Shannon made use of a tool developed by George Boole (1854) which he called logical algebra - now more commonly called Boolean Algebra.

Before considering the algebra consider the functions digital systems work with - introduce via T.T.

Most basic idea is that digital variables may have only two values - described by many choices of names:

0 and 1	Up and Down	Open and Closed
ON and OFF	True and False	High and Low etc

Most commonly used are 0,1 except in lab when using a logic probe - then use high, low or 5,0

Ordinary algebra - continuous variables - no end to the functions of the variables we can define; power series, polys., expon, trig ---- etc.

Algebra for digital systems - variables are binary variables i.e. have only two values \Rightarrow only a finite # of functions that can be defined (# may be large tho)


Functions of one binary variable $F(x)$;

x can only have values 0, 1

Any function of x can only have value 0, 1

So have four functions of one bin. var. as follows

x	$F_1(x)$	$F_2(x)$	$F_3(x)$	$F_4(x)$
0	0	0	1	1
1	0	1	0	1

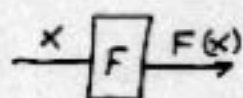

\uparrow Null Function $F_1(x) = 0$
 \Rightarrow short circuit

\uparrow x fnc $F_2(x) = x$

\uparrow NOT Function $F_3(x) = \bar{x}$
 or $= x'$
 or $= /x$

\uparrow Unit Function $F_4(x) = 1$
 tied to +

The new idea here is that of "negation" or the "complement" function. If $x=0$, then $\bar{x}=1$ and v.v., previously introduced as the "ganged" switch.

Functions of two binary variables: $F(x_1, x_2)$

By extrapolating above expect there will be a null function, a unit function, an x_1 function etc.

Certain of the functions are very important since they correspond to basic practical circuits (called primitive logic gates) and some are not of much interest in practical cases.

The functions are:

X_1	X_2	<u>Not OR</u>		F_3	F_4	<u>XOR</u>		F_8	F_9	<u>Not AND</u>		F_{10}	F_{11}	<u>AND</u>		F_{12}	F_{13}	<u>Not XOR</u>		F_{14}	F_{15}	<u>OR</u>	
X_1	X_2	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}	F_{16}	F_{17}	F_{18}	F_{19}	F_{20}	
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1

Functions we expected ↑

Important functions from table - have actual physical implementations:

F_8 function only when both inputs are simultaneously 1. This is the "AND" function and is generalized so that the AND of any # of variables is 1 only when all var. are 1.

F_7 is the complement of the AND.

Not AND called the "NAND" function

F_{14} function is a 1 when either x_1 or x_2 or both are 1. Called the "inclusive OR" function and often just called OR. Generalized to any # of inputs

F_1 is the complement of the OR.

Not OR called the NOR function or \overline{OR}


F_6 function is a 1 when either x_1 or x_2 is a 1 but not both. Called the XOR function where the X stands for exclusive. Also note it is a 1 when the inputs are different.

F_9 is the complement of the XOR. Usually written as \overline{XOR} . Note it is a 1 when inputs are the same.

Graphical symbols for gates:


Inverter

X	\bar{X}
0	1
1	0

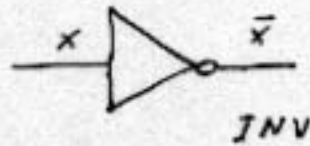


AND

X_1	X_2	F
0	0	0
0	1	0
1	0	0
1	1	1

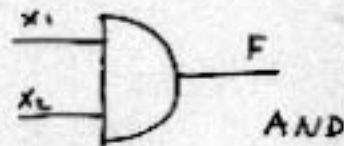

NAND

X_1	X_2	F
0	0	1
0	1	1
1	0	1
1	1	0

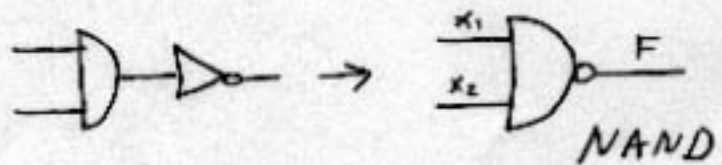


OR

X_1	X_2	F
0	0	0
0	1	1
1	0	1
1	1	1



NOR

X_1	X_2	F
0	0	1
0	1	0
1	0	0
1	1	0

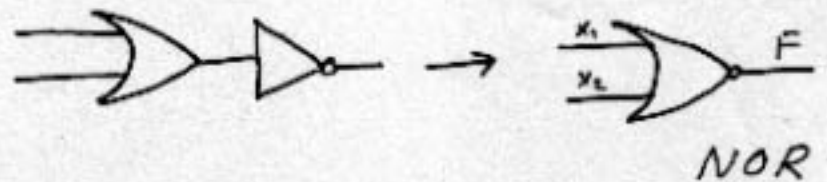


XOR

x_1	x_2	F
0	0	0
0	1	1
1	0	1
1	1	0



$\overline{\text{XOR}}$

x_1	x_2	F
0	0	1
0	1	0
1	0	0
1	1	1

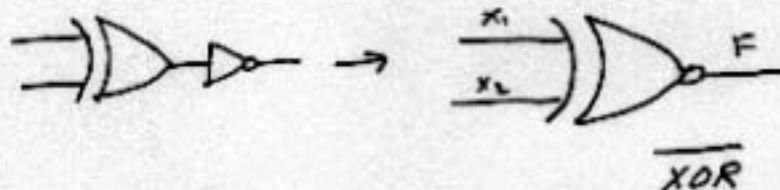

Functionally complete sets

Certain sets of the basic gates can realize any logic function. They include:

AND and INV

OR and INV

(Note inversion capability must be included)

NAND

NOR

↳ most common

Not going to try to list fnc's of 3 or more variables since:

# of var (N)	# states of the var (2^N)	# of functions (2^{2^N})
1	2	4
2	4	16
3	8	256
4	16	65,536

A

B

C

D


1

Symbols for common gates

2

3

4

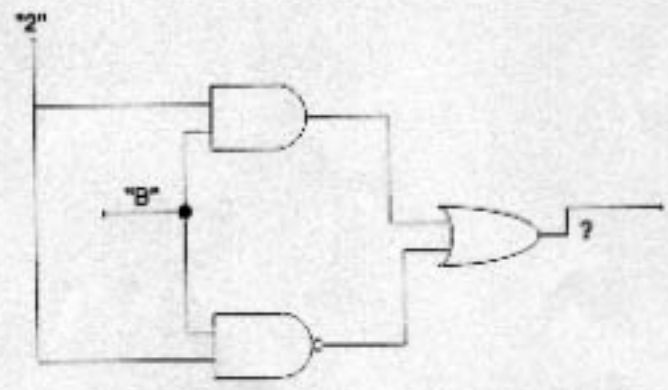**a simple logic circuit**

A

B

C

D

Boolean Algebra

Algebraic way of representing logic functions.

Boolean algebra defined by specifying elements, operations and a number of axioms or postulates.

Goes back to Shannon (1938) and back to Boole (1854).

E. Huntington (1904): his "first set of postulates" most commonly used to define two-valued Boolean algebra.

No need to go into the intricacies: need to define elements AS:

Binary variable: any variable can have only one of two values - call the values 0, 1

Define permitted operations and results of the operations

Three operations defined

- or ' or / Negation	• Logical Product	+ Logical Sum
$\overline{0} = 1$	$0 \cdot 0 = 0$	$0 + 0 = 0$
	$0 \cdot 1 = 0$	$0 + 1 = 1$
$\overline{1} = 0$	$1 \cdot 0 = 0$	$1 + 0 = 1$
	$1 \cdot 1 = 1$	$1 + 1 = 1$

Note there is no division or exponentiation etc as in "ordinary" algebra.

Note that the logical product "•" is the same as the AND function while logical sum is same as OR function.

Some useful theorems in Boolean Algebra

(Many are self-evident, some are not)

1. Zero and one rules:

$$0 + X = X$$

$$1 + X = 1$$

$$1 \cdot X = X$$

$$0 \cdot X = 0$$

2. Idempotent rules:

$$X + X = X$$

$$X \cdot X = X$$

3. Complementarity

$$X + \bar{X} = 1$$

$$X \cdot \bar{X} = 0$$

4. Involution

$$\overline{(\bar{X})} = \bar{\bar{X}} = X$$

5. Commutative

$$X + Y = Y + X$$

$$X \cdot Y = Y \cdot X$$

6. Associative

$$X + (Y + Z) = (X + Y) + Z$$

$$X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$$

7. Distributive

$$X \cdot (Y + Z) = X \cdot Y + X \cdot Z$$

$$(X + Y)(X + Z) = X + YZ$$

probably not obvious
take closer look

Proof by perfect induction: examine all possible states of LHS and show equal to RHS

			LHS			RHS		
X	Y	Z	X+Y	X+Z	(X+Y)(X+Z)	X	YZ	X+YZ
0	0	0	0	0	0 ✓	0	0	0 ✓
0	0	1	0	1	0 ✓	0	0	0 ✓
0	1	0	1	0	0 ✓	0	0	0 ✓
0	1	1	1	1	1 ✓ etc	0	1	1 ✓
1	0	0	1	1	1	1	0	1
1	0	1	1	1	1	1	0	1
1	1	0	1	1	1	1	0	1
1	1	1	1	1	1	1	1	1

LHS = RHS for all values of variables

8. Absorption laws (AKA subsuming)
(Useful in simplifying expressions)

$$X + XY = X \quad (X + XY = X \cdot 1 + XY = X(1+Y) = X)$$

$$X(X+Y) = X \quad (X(X+Y) = X \cdot X + X \cdot Y = X + XY = \text{above})$$

$$X + \bar{X}Y = X + Y \quad (X + \bar{X}Y = X(1+Y) + \bar{X}Y \\ = X + XY + \bar{X}Y = X + Y(X + \bar{X}) \\ = X + Y)$$