

Design Basics for Combinational Logic

first step: usually a word statement specifying what outputs for what inputs.

2nd step: Construct TT from statement. If there are any ambiguities in statement resolve them at this point.

3rd step: Develop "recipe" for the design by constructing either of two "standard forms" which are called the "Canonical Forms" (AKA transmission function).

Canonical form #1:

Rationale is to identify those input states which are to yield a 1 output, develop each of them in an AND gate and then sum.


input			out	Product Term
X	Y	Z	A	
0	0	0	1	$\bar{X}\bar{Y}\bar{Z}$
0	0	1	0	
0	1	0	1	$\bar{X}YZ$
0	1	1	0	
1	0	0	1	$X\bar{Y}\bar{Z}$
1	0	1	0	
1	1	0	1	$X\bar{Y}Z$
1	1	1	0	

List product term for each entry where A=1.

Product term has variable if it occurs as a 1, has the variable if it occurs as a 0. Then form sum;

$$\text{so: } A = \bar{x}\bar{y}\bar{z} + \bar{x}yz + xy\bar{z} + xyz$$

This is the recipe for the circuit:

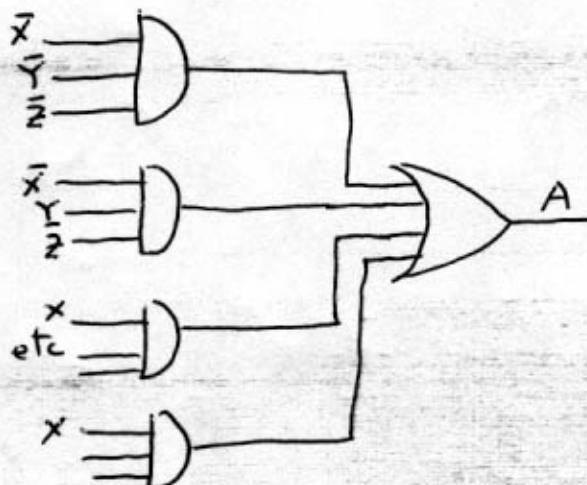

Called the "AND to OR" implementation

A here is called the "Sum of Products" or "SOP" Canonical Form.

Circuit above is correct and would work when built. However:

$$\text{Note: } A = \bar{x}\bar{z} \underbrace{(\bar{y}+y)}_1 + x\bar{z} \underbrace{(\bar{y}+y)}_1$$

$$= \bar{x}\bar{z} + x\bar{z}$$

$$= \bar{z}(\bar{x}+x)$$

$$\text{so } A = \bar{z}$$

ckt is

moral: it often pays to see if expression has any obvious simplification.


Canonical form #2

Identify input states which are to yield a 0 output.
 For each, form sum of input variables - uncomplemented if entry is a 0, complemented if entry is a 1.
 Then form product of each such sum term.

X	Y	Z	A	Sum Term
0	0	0	1	
0	0	1	0	$X + Y + \bar{Z}$
0	1	0	1	
0	1	1	0	$X + \bar{Y} + \bar{Z}$
1	0	0	1	
1	0	1	0	$\bar{X} + Y + \bar{Z}$
1	1	0	1	
1	1	1	0	$\bar{X} + \bar{Y} + \bar{Z}$

$$\text{so: } A = (X + Y + \bar{Z})(X + \bar{Y} + \bar{Z})(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + \bar{Z})$$

This is recipe for circuit:

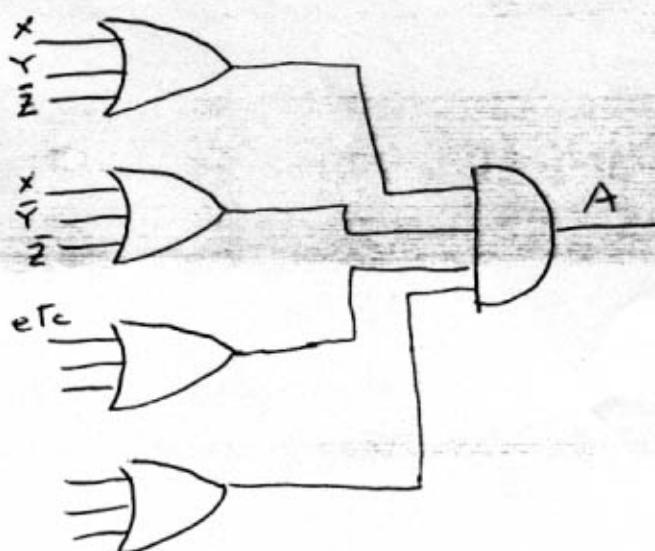

Called the "OR to AND" implementation.

A here is the
"Canonical Product of
Sums" or POS Form.

Home exercise: Show A here again reduces to $A = \bar{Z}$

Additional nomenclature:

A "literal" is the appearance of a variable in either true or complemented form.

- For SOP form, each term is called a "min-term" and corresponds to a row in the TT.

Given a SOP write the literals in each term in same order. Assign binary digit to each literal, 0 if appears uncomplemented, 1 if appears complemented here:

$$A = \underbrace{\bar{X} \bar{Y} \bar{Z}}_{000} + \underbrace{\bar{X} Y \bar{Z}}_{010} + \underbrace{X \bar{Y} \bar{Z}}_{100} + \underbrace{X Y \bar{Z}}_{110}$$

$m_0 \quad m_2 \quad m_4 \quad m_6 \leftarrow$ the min-terms

$0, 2, 4, 6$ = dec. equiv.

hence express $A = \sum m(0, 2, 4, 6)$
in min-term form

- For POS form: assign binary digit to each literal in each sum term - 0 if appears uncomplemented, 1 if appears complemented

here: $A = \underbrace{(X + Y + Z)}_{001} (\underbrace{X + \bar{Y} + \bar{Z}}_{011}) (\underbrace{\bar{X} + Y + \bar{Z}}_{101}) (\underbrace{\bar{X} + \bar{Y} + \bar{Z}}_{111})$

$M_1 \quad M_3 \quad M_5 \quad M_7$

These are
"Max-terms"


hence express $A = \prod M(1, 3, 5, 7)$ $\prod \Rightarrow$ continuous product
in Max-term form

Summarize →

row #	X	Y	Z	A	SOP product terms	POS sum terms	min terms	Max terms
0	0	0	0	1	$\bar{X}\bar{Y}\bar{Z}$		m_0	
1	0	0	1	0		$X+Y+\bar{Z}$		M_1
2	0	1	0	1	$\bar{X}Y\bar{Z}$		m_2	
3	0	1	1	0		$X+Y+\bar{Z}$		M_3
4	1	0	0	1	$X\bar{Y}\bar{Z}$		m_4	
5	1	0	1	0		$\bar{X}+Y+\bar{Z}$		M_5
6	1	1	0	1	$X\bar{Y}\bar{Z}$		m_6	
7	1	1	1	0		$\bar{X}+Y+Z$		M_7

Now have basic tools for both analysis and synthesis of combinational logic circuits.

Analysis straight forward, e.g.

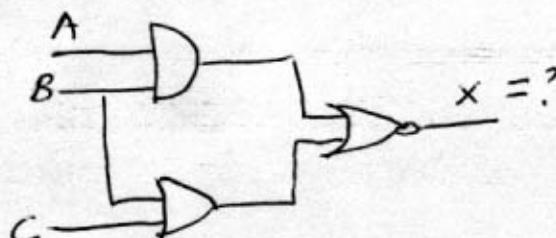

$$x = \overline{A \cdot B + (B+C)} \text{ directly, but good idea to try to simplify}$$

$$x = (\overline{A} \cdot \overline{B})(\overline{B} + C) = (\overline{A} + \overline{B})(\overline{B} \cdot C)$$

$$= \overline{A} \overline{B} \bar{C} + \overline{B} \overline{B} \bar{C}$$

$$= \overline{A} \overline{B} \bar{C} + \overline{B} \bar{C}$$

$$= \bar{B} \bar{C} (\bar{A} + 1)$$

$$= \bar{B} \bar{C}$$