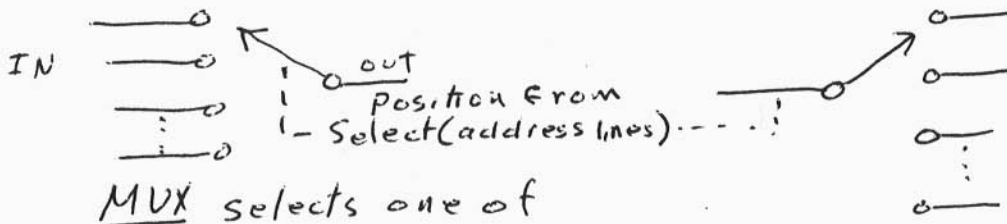


# Demultiplexer


Opposite of MUX.




MUX selects one of many inputs

DMUX connects one input to one of many outputs.

 Note MUX's and DMUX's are special forms of encoders and decoders which are circuits characterized by



 e.g. a BCD to Decimal decoder  
(form of DMUX)




e.g. 8 bit # in  
2 bits out to say input # is either prime or divisible by, say, 7.  
(form of MUX)


Representative DMUX's

- 74155 dual 1 to 4
- 74139 1 to 8
- 74154 1 to 16

Symbol:

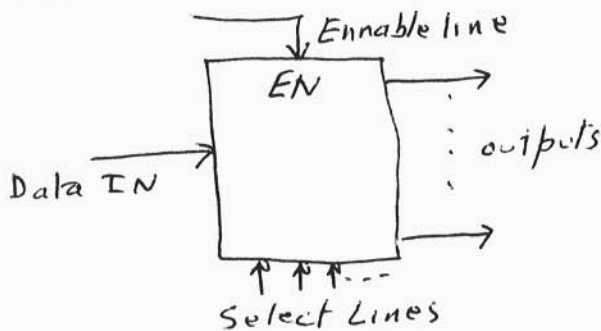

## An application:

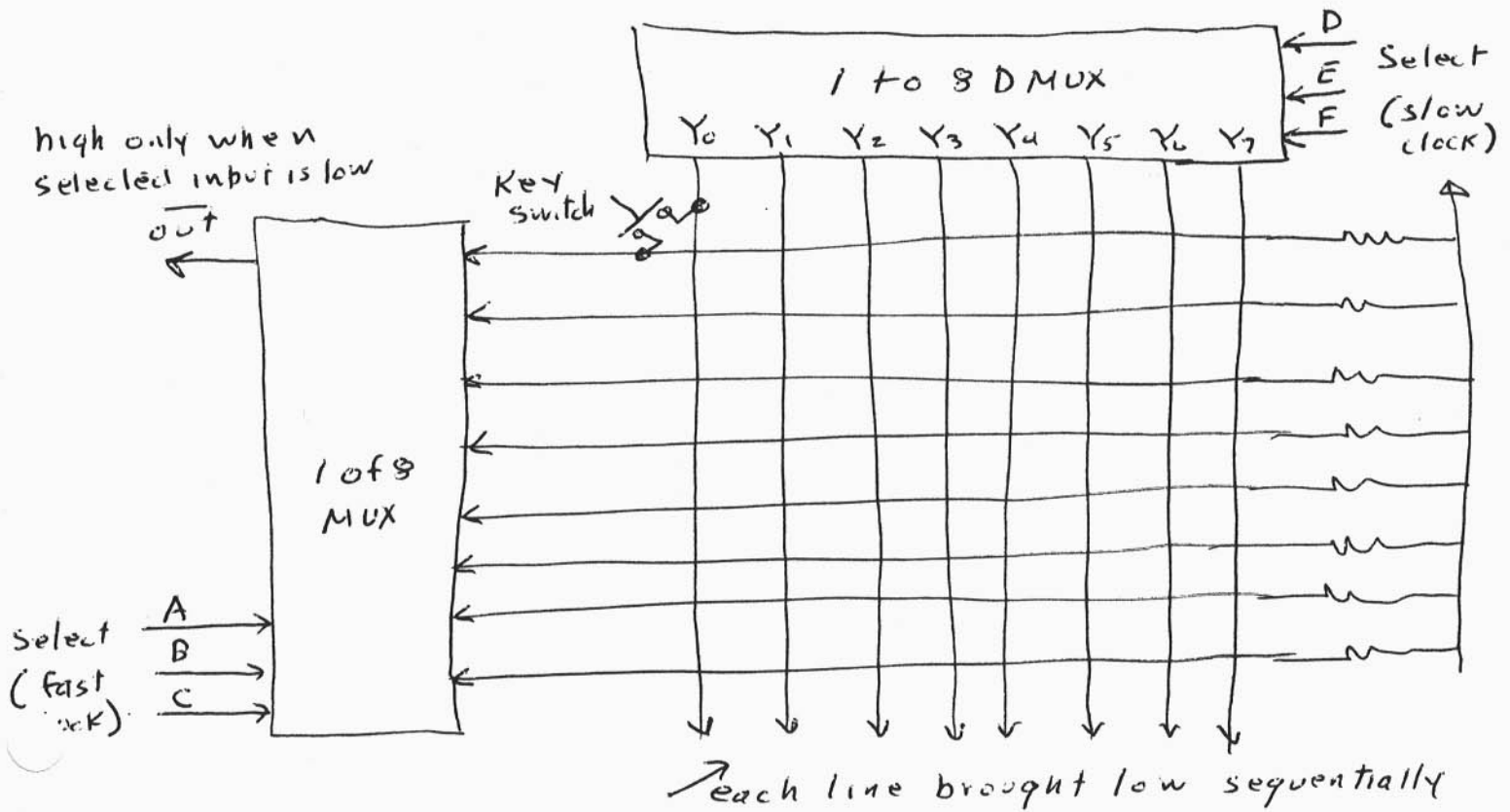

One Key switch at each row/column intersection,

DEF selects one output of the DMUX and brings it low so that column is low.

If a key has been depressed then one of the rows is connected to that column.

Scan (rapidly) the rows to find which row/column key has been depressed (when find it out will go high).

Then ABCDEF (6 bits) uniquely define the key.

Hence have a 64 keypad encoder here.

## Sequential Circuits - Basics

Circuits studied so far have been "combinational logic circuits" - circuits whose output(s) is determined solely by its present inputs. What has gone on in the past has no bearing on what is happening now.

Sequential logic circuits have outputs which depend not only on present inputs but also, to a greater or lesser extent, on what has happened in the past, i.e. they have memory in one form or another. Some examples of applications include:


1. Latching; involves acquiring and holding on to states of a circuit at a particular time.
2. Parallel to serial and vice versa conversion.
3. Serialization of operations.
4. Counting of events
5. Sequencing of events.

### The "Latch"

For comb. logic there are a small # of primitive logic gates (just one?) which can be combined and packaged to implement higher order functions.


Same thing is true for sequential circuits. The primitive device is the "latch", which is sometimes called a "bi-stable".

Consider:

 


one inverter + f.b.

Two constraints

 


condition for both constraints satisfied,

Now consider:

 

 stays 1 0 1  
2 inverters + f.b.  
or 0 1 0




Condition both constraints satisfied yields 3 pts, two of which are "stable" and one is "unstable".

Stable  $\Rightarrow$  ckt can remain there indefinitely until told to go to other S pt.

Unstable  $\Rightarrow$  ckt cannot stay there - will oscillate about this pt: topic for a more advanced electronics course,

As shown only way to change state is to bring appropriate point to +5 or gnd.

 
More practical implement the inverters with NOR or NAND gates




$$(\overline{A+B} = \overline{A} \text{ if } B=0)$$

Now make use of the inputs:

# NOR type latch:

 

usually drawn as

 

Note have feedback: characteristic of sequential but not of comb. logic ckts.

NOR gates impose conditions on the 4 quantities; i.e. must satisfy:

$$Q' = \overline{S+Q} \quad Q = \overline{R+Q'}$$

Check all possible states to determine those which are self-consistent: e.g.

S	R	Q	Q'	
0	0	0	0	← is $Q = \overline{0+0} = 1$ ? No good x
0	0	0	1	← is $Q = \overline{0+1} = 0$ , and $Q' = \overline{0+0} = 1$ ? Yes - self con state

By going thru all possibilities end up with table:

S	R	Q	Q'	
0	0	0	1	} idle
0	0	1	0	
0	1	0	1	} reset
1	0	1	0	} set
1	1	0	0	} disallowed

Comments re table:

- States marked "idle" correspond to initial ckt with only inverters: outputs may be 1,0 or 0,1 depending on history.

2. If  $S, R = 0, 1$  then  $Q$  is forced to 0 and the latch is said to be "Reset".
3. If  $S, R = 1, 0$ , then  $Q$  is forced to 1 and the latch is said to be "Set".
4. The condition where  $S=1=R$  is not allowed, although if it obtains both  $Q$  and  $Q'$  are both forced to 0. Not allowed since if we were to go to idle state ( $S=0=R$ ) then can't predict if  $Q, Q'$  would be 1, 0 or 0, 1 as determined by intermediate stage  $S, R = 0, 1$  or  $1, 0$ .
5. Idle state: AKA resting state, inactive state, do nothing state, memory state, or quiescent state.
6. Except for disallowed state,  $Q$  and  $Q'$  are complements and can be written as  $Q, \bar{Q}$ , which is commonly done (with caveat).

Characteristic table:

Previous table can be simplified a bit by writing it as:

S	R	$Q_{n+1}$
0	0	$Q_n$ no change idle,
0	1	0 reset
1	0	1 set
1	1	not allow (0, 0)

$S =$  set input,  $R =$  reset input

$Q_n =$  output before input change



$Q_{n+1} =$  " after " "

Assumes both  $Q$  and  $\bar{Q}$



### NAND type latch:

Fairly obvious that instead of using NOR with 1 input 0 as an inverter, could use NAND with 1 input 1 as an inverter. Dual development follows, summarized as  $\rightarrow$

## NOR Latch

  

## NAND Latch

  

S	R	Q	Q'
0	0	0	1
0	0	1	0
0	1	0	1
1	0	1	0
1	1	0	0

idle (for 0,0 and 0,0)  
reset (for 0,1)  
set (for 1,0)  
disallowed (for 1,1)

S	R	Q	Q'
0	0	1	1
0	1	0	1
1	0	1	0
1	1	0	1
1	1	1	0

disallowed (for 0,0 and 1,1)  
reset (for 0,1)  
set (for 1,0)  
idle (for 1,1)


## char table

S	R	Q <sub>n+1</sub>
0	0	Q <sub>n</sub> idle
0	1	0 reset
1	0	1 set
1	1	(0,0) dis

## char table


S	R	Q <sub>n+1</sub>
1	1	Q <sub>n</sub> idle
0	1	0 reset
1	0	1 set
0	0	(1,1) dis.

 to get same char table put inver in front of NAND input





S	R	Q <sub>n+1</sub>
0	0	Q <sub>n</sub> (former S=R=1)
0	1	1 (former S=1, R=0) ←
1	0	0 (former S=0, R=1) ←
1	1	1,1 dis (former S=0, R=0)

 now 0,0 is idle and 1,1 is S. but 0,1, 1,0 states are complements of NOR, so just relabel (ie switch outputs)



now NOR char table is generic

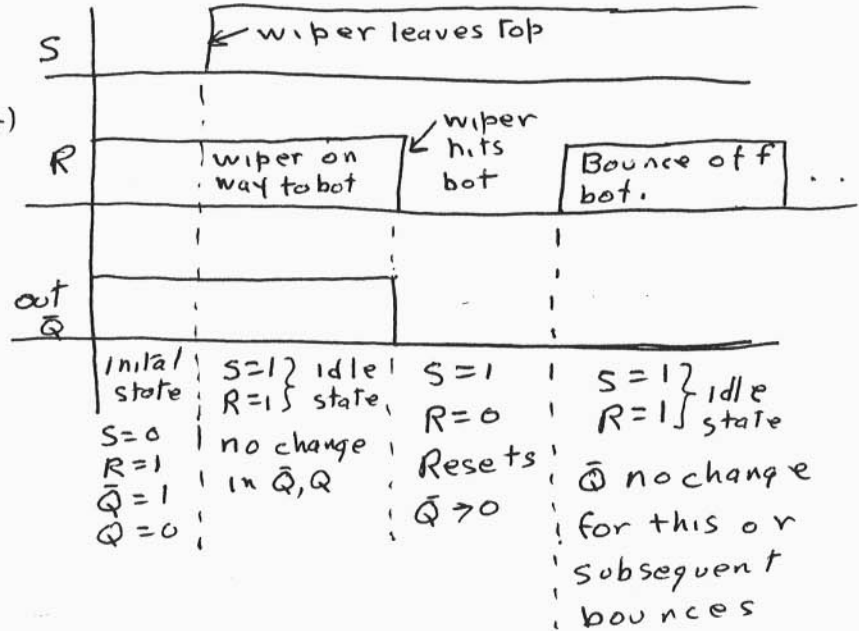 
Application of a simple latch = switch debouncer. Ordinary switches are commonly used to input into logic ckts. Many suffer from "bounce" (i.e. actually physically bounce on the contact point). Can cause extraneous inputs. Debouncer used:



Controlled latches = S-R (or R-S) Flip-Flops

Latches so far have no controlling inputs other than their S-R inputs and are therefore always ready to respond to changes in S, R: they are termed "transparent". Most often we want them to be operative (enabled) only at specific times. Done by adding another input to gate the primary inputs: e.g.

Gated NOR latch:

 

If line Cp is high, then S, R have their usual effect on Q.

If Cp is low, then inputs to NOR's are brought low = idle state and no change in  $\bar{Q}, Q$  permitted regardless of what S, R are.




## Types of $C_p$ :

1. Most common:  $C_p$  is the system clock, latch (F-F) can respond any time clock is high.
2. Strobe:  $C_p$  is a pulse whose ON time is short w/r to system clock, Enables F-F for brief time.
3. Gate:  $C_p$  is a pulse whose ON time is long w/r to system clock. Not very common.

 
## Synchronizing feature of S,R FF (i.e. clocked latch):

Assume S, R coming in from outside. FF can only respond when  $C_p$  is high.

(Note still can't have S, R high at same time)




## Gated NAND latch: same deal

 

$C_p$  high  $\Rightarrow$  normal operation  
 $C_p$  low  $\Rightarrow$  latch proper forced to idle state, no change permitted.

 Data type latch (F-F): a common use of a gated latch is to acquire and retain state of a logic line at a given instant.  $C_p$  used may be clock or a strobe depending on application. Inverter used so that S and R are always complements.



Need as many of these as there are D lines:

Naturally never build - instead buy, e.g.

7475 = 4 bit latch (~50¢)

74100 = 8 " (i.e. "octal") latch (~1.25)

and an even more versatile one

74LS373 (~1.35) = an "octal D type transparent latch with tri-state outputs"

A tri-state output has a special enabling line which either causes the output to behave normally or, in effect, disconnects it from whatever it was driving. Very useful and quite common feature.