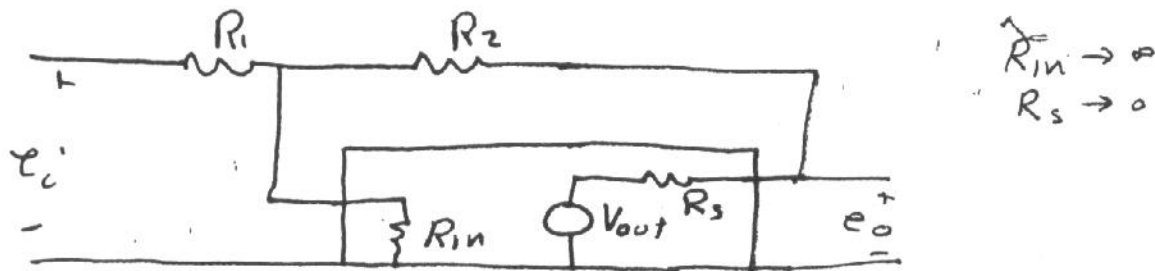


Assumption here was that adding the amplifier did not "load" the point ϵ nor having to supply current did not change the amplifier's output. In terms of the VCVS model:



From preceding the characteristics which make an amplifier an "operational amplifier" are:


Feature	Ideal	Practical values
"Raw" Gain G	∞	$10^4 \rightarrow 10^7$
Input resistance R_{in}	∞	$10^5 \rightarrow 10^9$
Input current implied by R_{in}	0	$.1 \text{ ma} \rightarrow 10^{-9}$
Output resistance R_s	0	$100 \rightarrow 1000$
Other features not apparent from preceding:		
Bandwidth	∞	large enough for job
DC drift	$0 / ^\circ\text{C}$	$1 \text{ mv}/^\circ\text{C} \rightarrow .001 \text{ mv}/^\circ\text{C}$

Cost of the amplifiers range from 50¢ to \$50 depending on special features such as high power output capability.

- Golden rules } 1. Amplifier draws no current
 2. " input is at 0 potential

Typical instrumentation applications:


1. Basic:

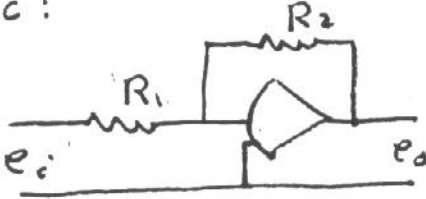

$$e_o = -\frac{R_2}{R_1} e_i$$

- $R_2 > R_1$ amplifier
- $R_2 = R_1$ inverter
- $R_2 < R_1$ active attenuator

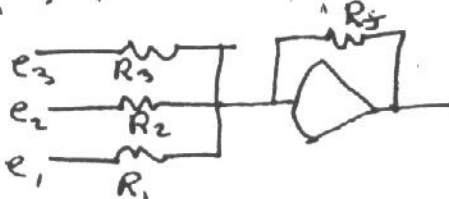2. Weighted summer (basic idea behind D/A converters)




$$e_o = -\left[\frac{R_f}{R_1} e_1 + \frac{R_f}{R_2} e_2 + \dots \right]$$

each channel

can have separate scale factor

One of the inputs can be used for offset control.

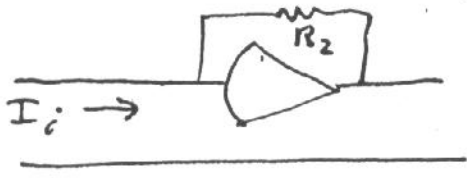
3. Current measuring (current to voltage transduction)



$$e_o = -R_2(I_i)$$

ideal ammeter measures I_i

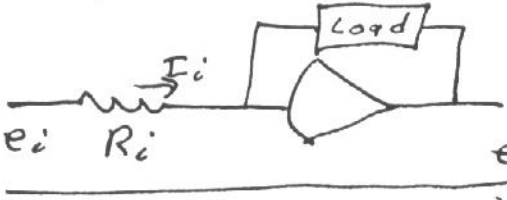4. Current controlling (measure V-I characteristic of non-linear device, e.g. diodes)




force $I_i = \frac{e_i}{R_i}$ through the load

$$e_o = -V_{device}(I_{device})$$

Basic idea of Tektronik curve tracer

5. Differentiator

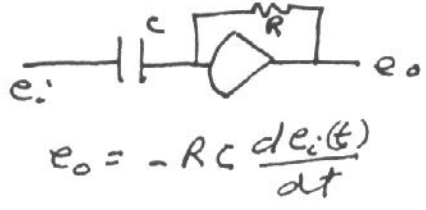

$$e_o = -RC \frac{de_i(t)}{dt}$$

6. Integrator




$$e_o = -\frac{1}{RC} \int e_i(t) dt$$

Differential amplifier: OPA actually have two inputs with

output given by:  $e_0 = A(e_+ - e_-)$

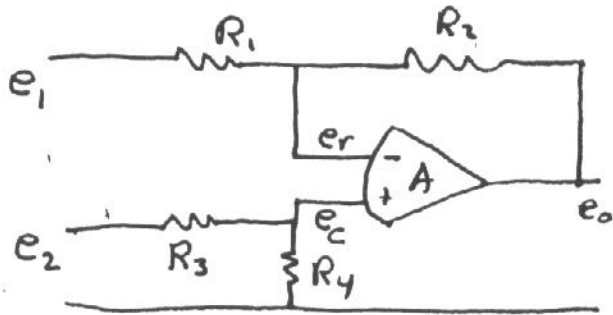In preceding the "+" input was assumed grounded.



$$e_0 = A(e_+ - e_-)$$

$$e_+ = \frac{R_4}{R_3 + R_4} e_2$$

$$e_- = \frac{R_1}{R_1 + R_2} e_0 + \frac{R_2}{R_1 + R_2} e_1$$

$$e_0 = A \left[\frac{R_4}{R_3 + R_4} e_2 - \frac{R_1}{R_1 + R_2} e_0 - \frac{R_2}{R_1 + R_2} e_1 \right]$$

Solve for e_0 : can put in form when take $A \rightarrow$ large

$$e_0 = -\frac{R_2}{R_1} e_1 + \frac{R_2}{R_1} \frac{1 + \frac{R_1}{R_2}}{1 + \frac{R_3}{R_4}} e_2$$

set $\frac{R_1}{R_2} = \frac{R_3}{R_4}$ (condition for a "differential" amplifier)

to get $e_0 = \frac{R_2}{R_1} (e_2 - e_1)$ (useful for balanced to unbalanced

conversion such as when inputs are from a bridge.

If solve for e_+ find it = e_- = generalized


virtual ground concept i.e. differential input to

amp = 0 (i.e. $e_+ = e_-$ in ideal case of large A)

Special cases:

1) Let $R_3 \rightarrow 0$ output reduces to $e_o = -\frac{R_2}{R_1} e_1 + \left(1 + \frac{R_2}{R_1}\right) e_2$

Note that then R_4 is incidental so have

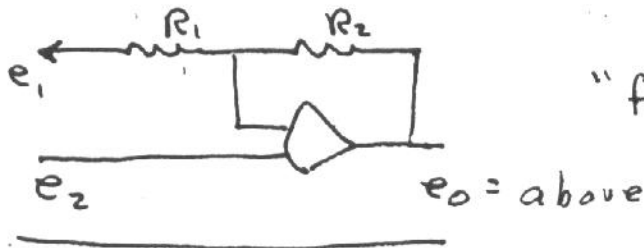

"follower with gain and offset control"

(Very useful ckt)

e_1 can of course be set to 0 if not needed

source of e_2 sees no loading i.e. is "buffered"


2) If now set $R_2 = 0, e_1 = 0$ (then R_1 is incidental) get "unity gain buffer" stage



(simplest ckt since no R's involved)

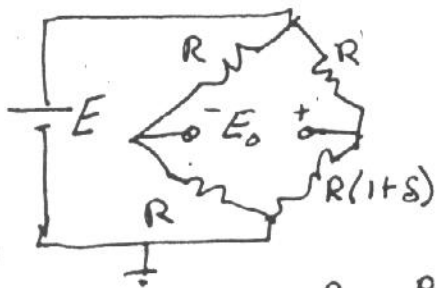
3. Linearized bridge:

Say have element whose resistance is $R(1+s)$ where s is deviation from reference (eg a temp dependent device) Used in a bridge



$$E_o = \left[\frac{R(1+s)}{R + R(1+s)} - \frac{1}{2} \right] E_{in} = \frac{s}{2(2+s)} E_{in}$$


= nonlinear in s
instead use:

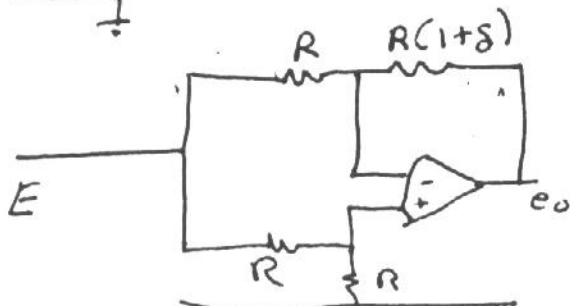

$$\begin{aligned} e_o &= E \left(\frac{1}{2} \right) \left(1 + \frac{R(1+s)}{R} \right) - \frac{R(1+s)}{R} E \\ &= \left[\frac{1}{2}(1+s) - (1+s) \right] E \\ &= E \cdot \frac{s}{2} = \text{linear in } s \end{aligned}$$

Instrumentation amplifier: readily available now and at reasonable cost (\$6-\$20)

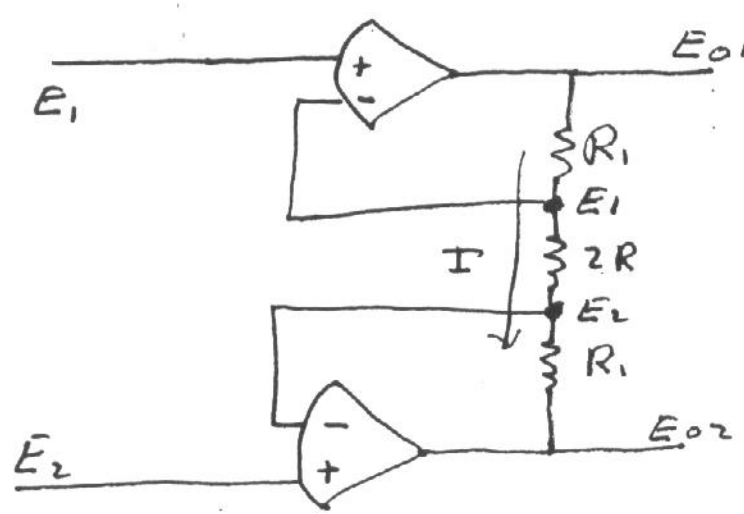Combines buffering with differential action:



$$I = \frac{E_1 - E_2}{2R}$$

$$E_{01} = E_1 + I R_1 = E_1 + \frac{R_1}{2R} (E_1 - E_2)$$


$$E_{01} = E_1 \left(1 + \frac{R_1}{2R}\right) - \frac{R_1}{2R} E_2$$

similarly get

$$E_{02} = E_2 - I R_1 \text{ which gives}$$

$$E_{02} = E_2 \left(1 + \frac{R_1}{2R}\right) - \frac{R_1}{2R} E_1$$

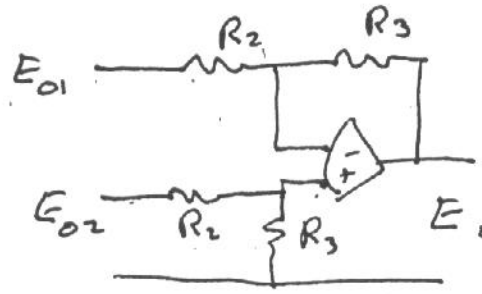put E_{01}, E_{02} into a standard dif. amp stage



$$E_0 = - \frac{R_3}{R_2} \left(1 + \frac{R_1}{R}\right) (E_2 - E_1)$$


All above put in one package with R brought out to set gain.

(Very useful ckt)

Note both inputs buffered, gain set with one R.

Some non-linear OA applications

Diode limiter - soft

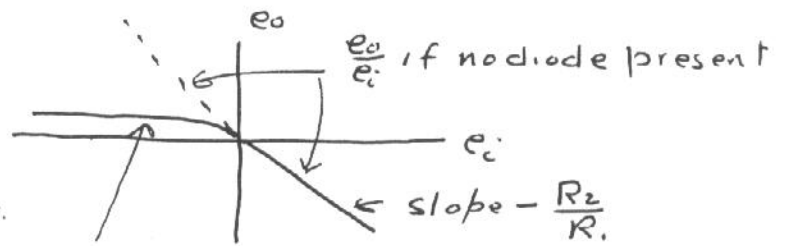


as output tries to go +ve diode conducts, slope then $\sim \frac{R_2 \parallel R_2}{R_1}$

reverse diode to get limiting in other direction.


Diode limiter - hard

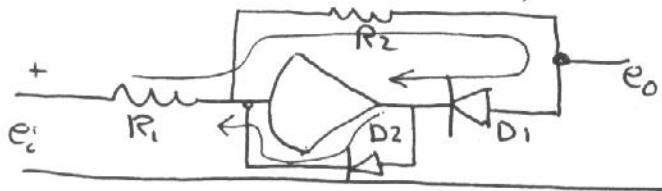Improve characteristic by putting diode inside the f.b. loop and taking output as shown:



$$e_o = -\frac{R_2}{R_1} e_i = -R_2 \left(\frac{e_i}{R_1} \right) \text{ as long as } D_1 \text{ is conducting (current direction as shown).}$$

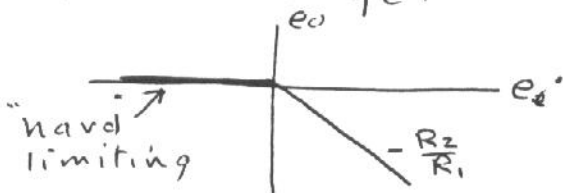D_2 needed to provide path for current in opposite direction to avoid amplifier going into saturation. for above get




if reverse both diodes get




Variable level limiting

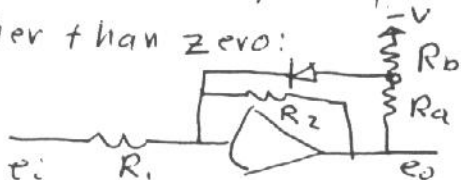By adding couple resistors can get limiting to occur at other than zero:




home exercise


show that get

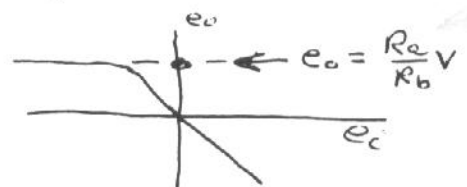

The 11 circuit:

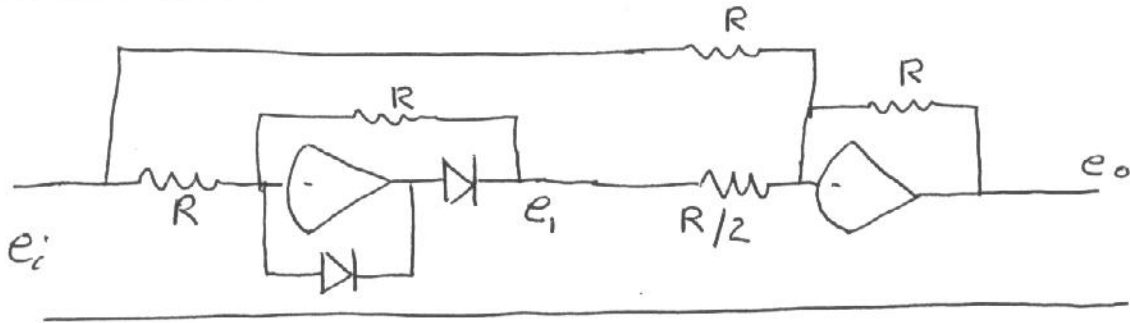


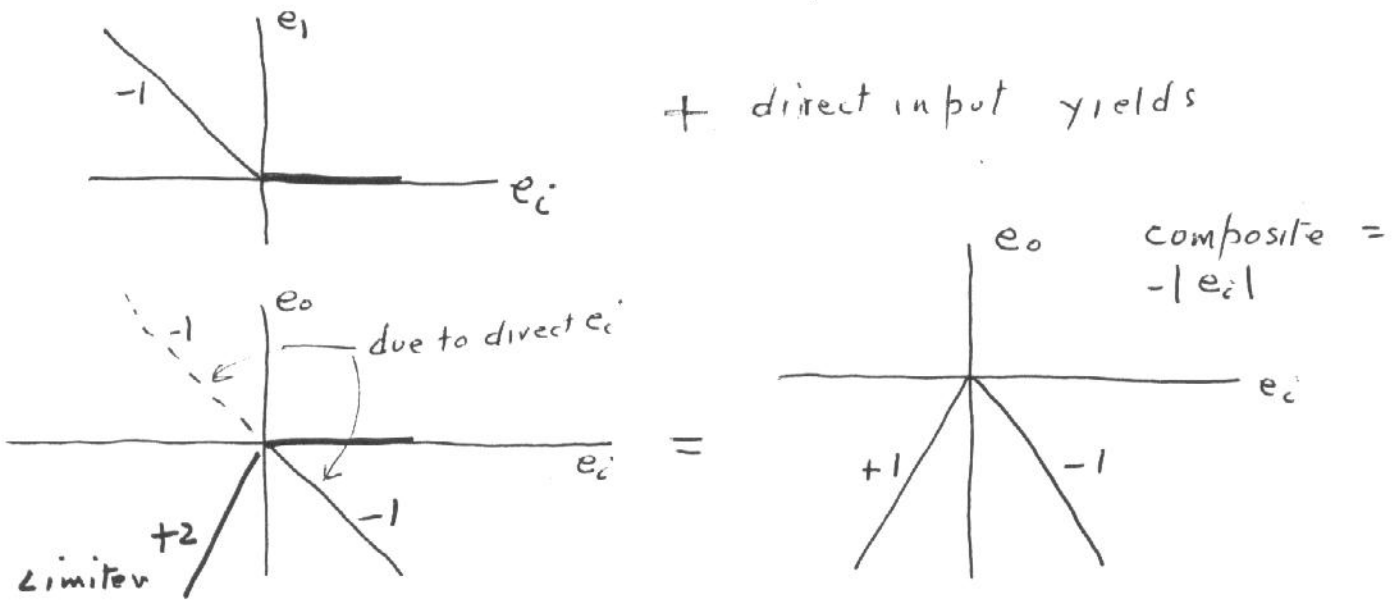Note that output amplifier sums $-1 \cdot e_i - 2 \cdot e_1$ and that e_1 is a hard limiter, i.e.




Circuit is also called a precision rectifier. Can add an inverter to get +11. Can be used as front end to A/D converter or DMM which want unipolar inputs.

Precision Rectifier

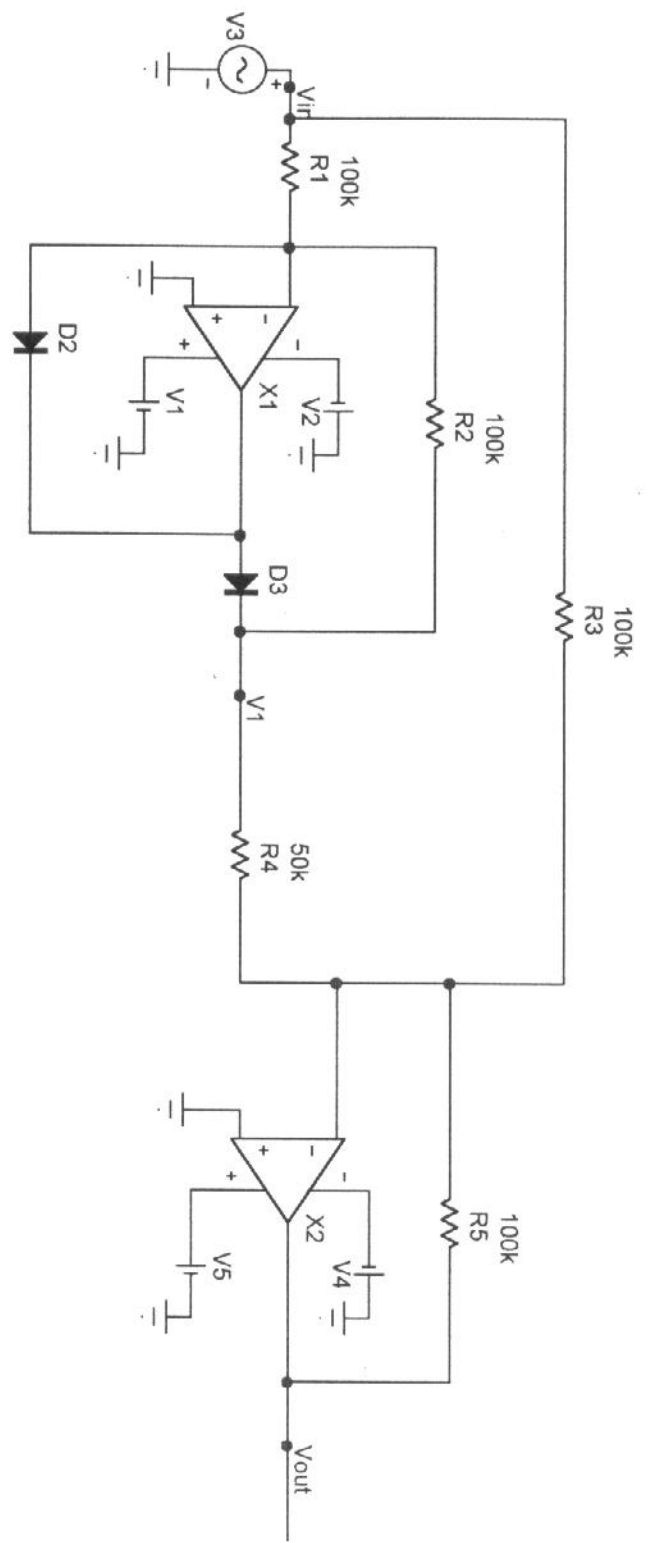

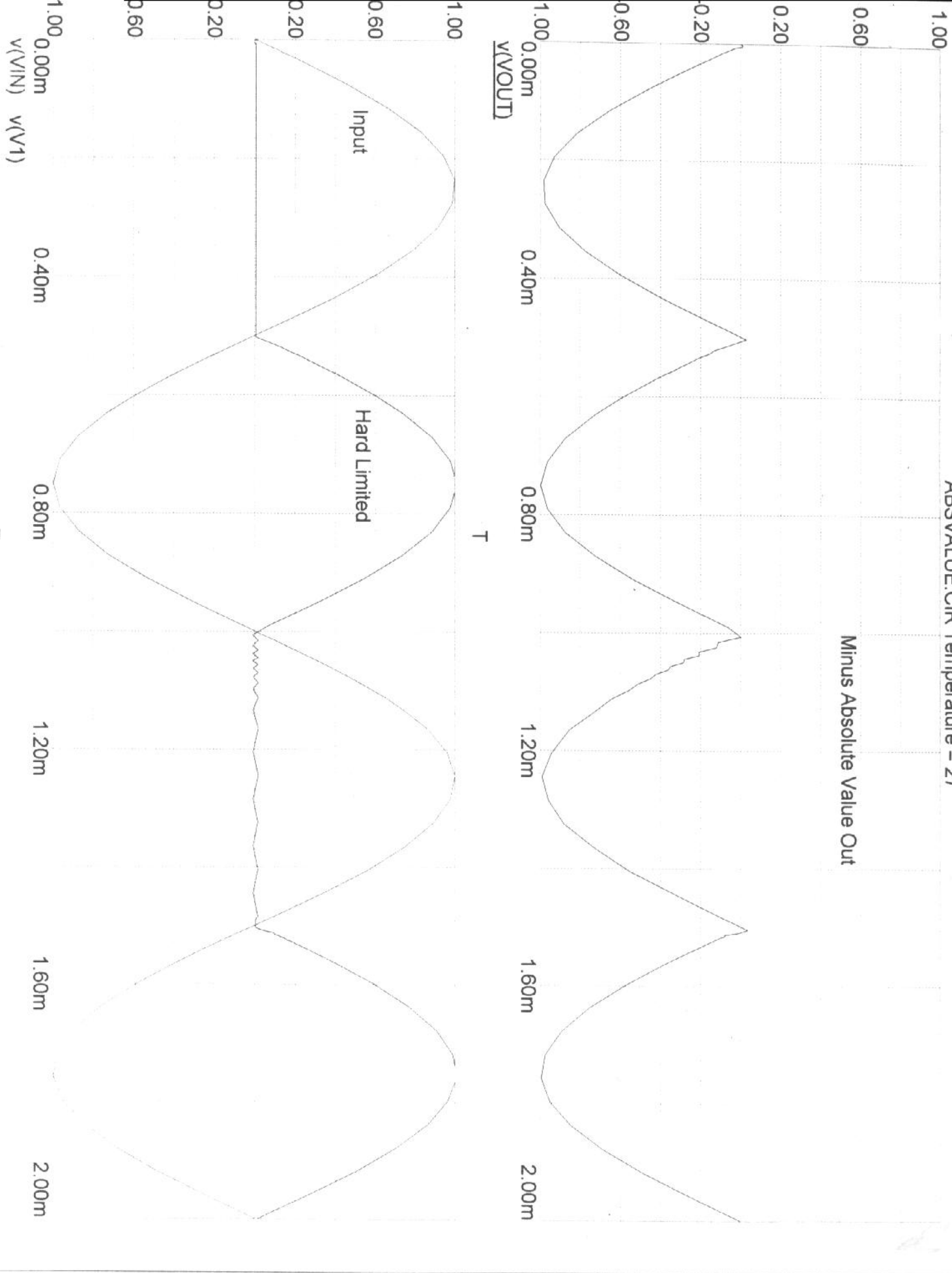
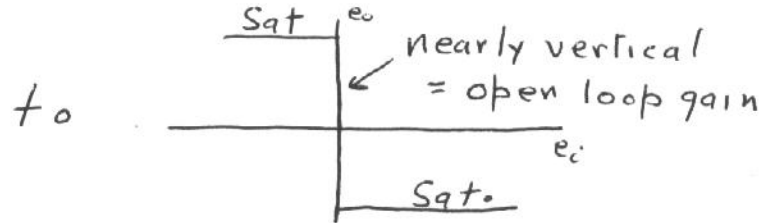
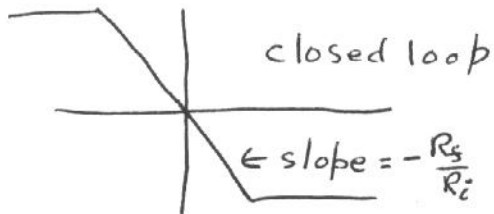
ABSVALUE.CIR Temperature = 27

Minus Absolute Value Out




Comparators (AKA zero crossing detectors, level detector)

for  as $R_f \rightarrow \infty$, $\frac{e_o}{e_i}$ goes from



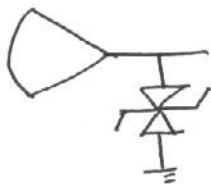
Saturation level could be left to amplifier to decide or set by back-to-back Zener diodes



Zener diodes use well defined reverse breakdown





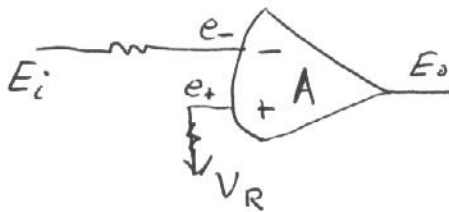Using open loop OA and reference voltages get following types of operation:




$$E_o = A(e_+ - e_-)$$


$$= A(V_R - E_i)$$

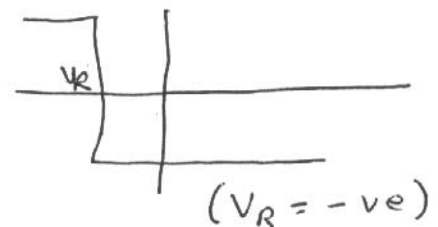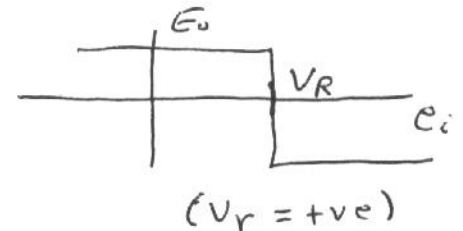

or

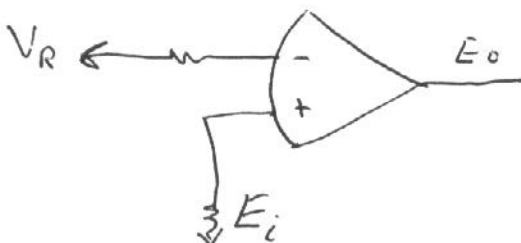

$$E_o = A(E_i - V_R)$$

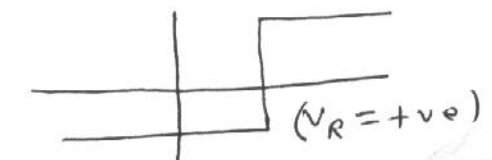


Comparator as indicated above have two issues to be addressed in practice:

1. Ordinary OA's would use $\pm 15V$ power supplies giving saturation values that are bipolar, i.e. + and - values, either set by the OA itself or by clamping diodes. Not suitable if output is to drive digital logic ckts. Could be handled by another OA used as a level shifter but in practice manufacturers design from beginning to use single, +5V, supplies with internal clamping so that output sat values are $\approx 0, +5V$.

Hence there are many IC's designated as comparators accepting analog inputs and outputting standard logic levels.


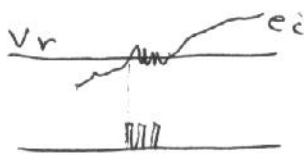
2. Chatter (AKA squegging or jitter): If the input has noise spikes on it will get multiple, unwanted, state transitions.



Depending on the application may or may not be serious: e.g. turning on sump pump when water level rises - not a problem probably.

Counting process events - probably a problem.

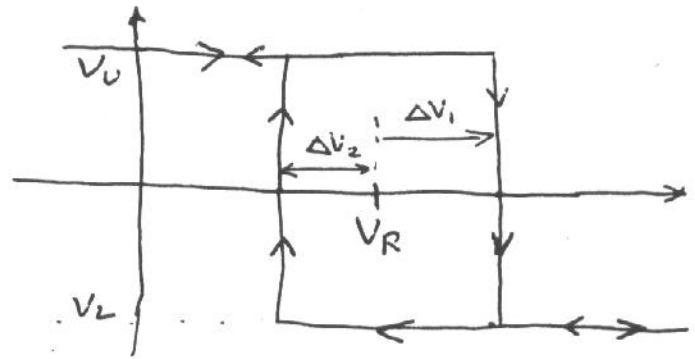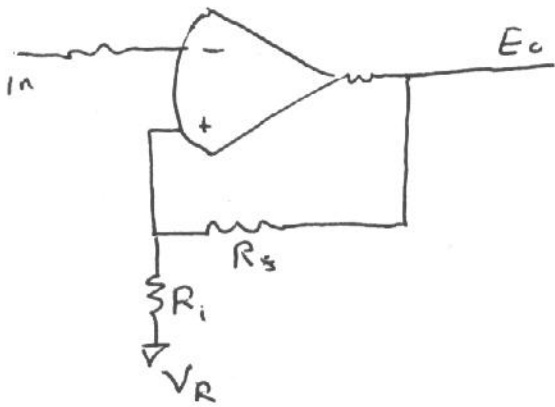Common way out is to insert hysteresis (= automatic modification of the threshold (i.e. V_r) level) via a little feedback. A small increment is added to the reference when the output is "high" and subtracted from the reference when the output is "low".



When output is positive the fixed reference V_R is modified to $V_R + \Delta V_1$, with $\Delta V_1 = \frac{R_i}{R_i + R_s} V_U$

When output is negative, fixed reference modified to $V_R - \Delta V_2$ where $\Delta V_2 = \frac{R_i}{R_i + R_s} V_L$

Note: approximation used that $R_s \gg R_i$, as is usually the case. Actual values of hysteresis in practice range from mV to fractions of a volt.

Packaged units available (eg 7413) and usually have symbol like



7413 has built in hysteresis of $\approx 0.4V$.

